
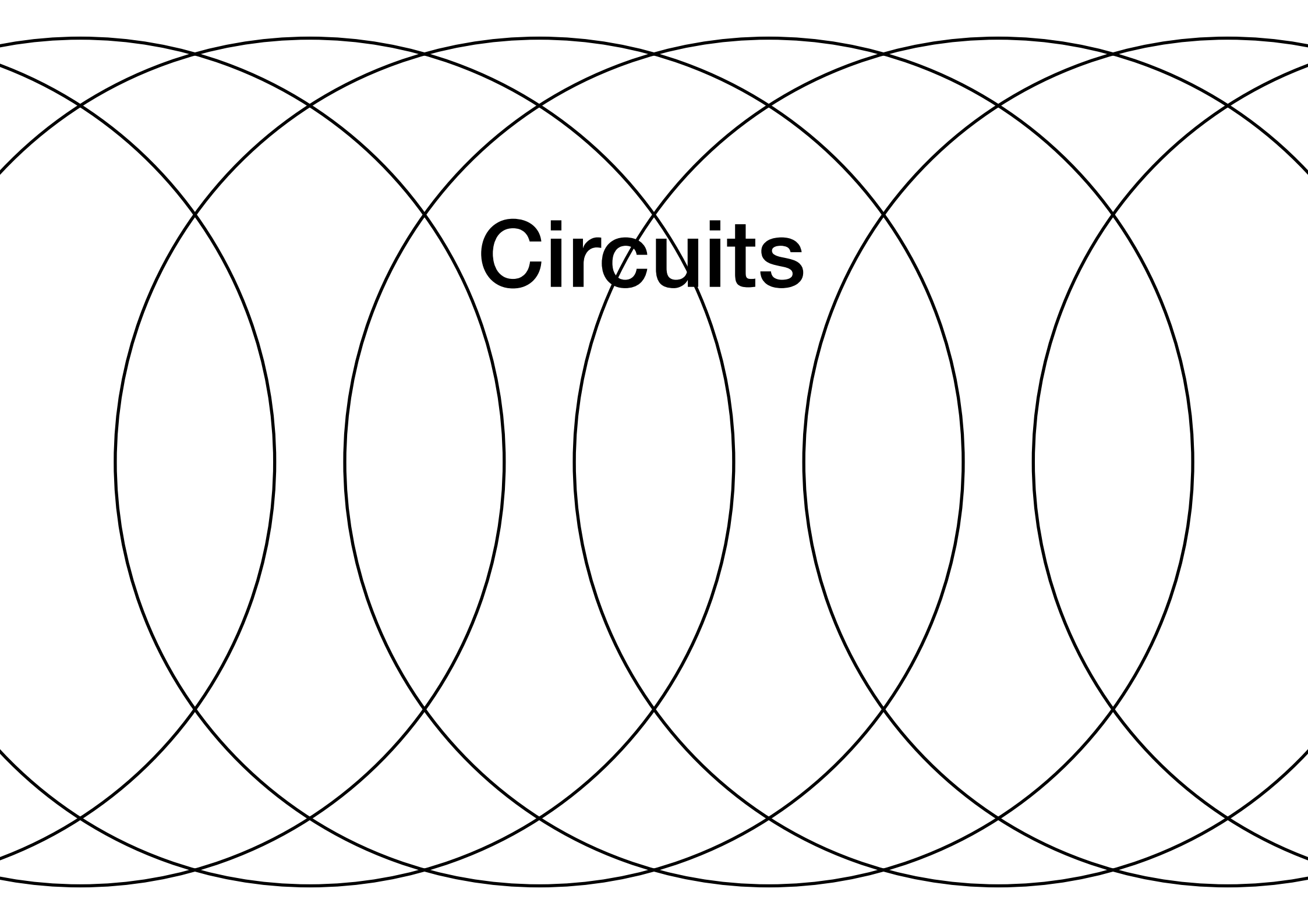


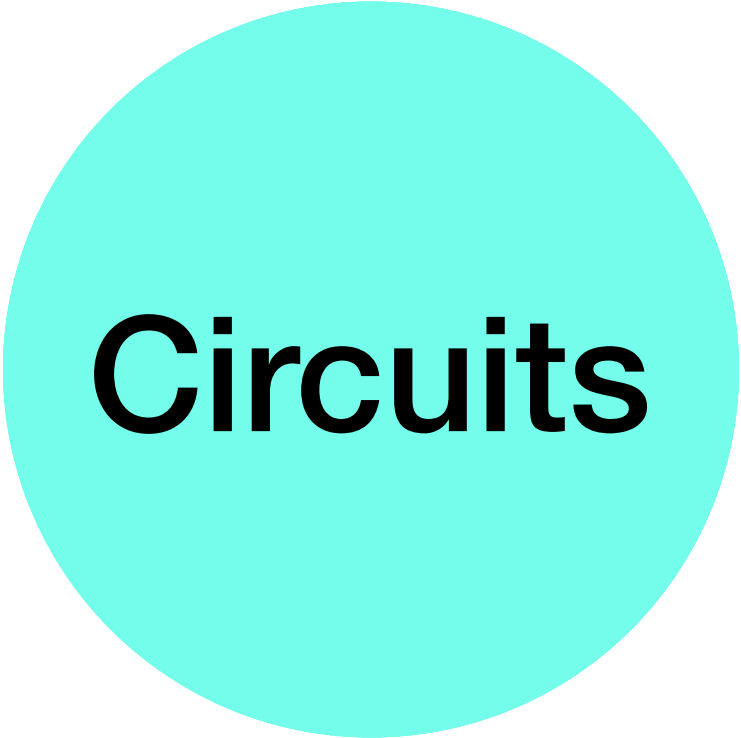

Circuits



Circuits


Introduction

Some materials contain charged particles which are free to move around, for example metals contain free electrons.

If we connect a battery to a metal these electrons will flow in a loop from one side of the battery to the other. We call this flow of charge an electrical current. We call the loop a circuit.

Current (I)

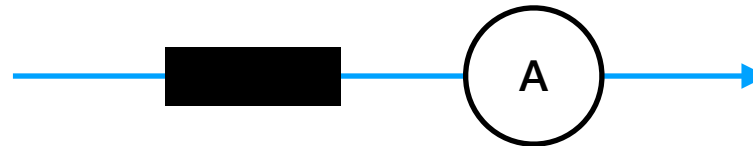an ammeter shows the
current flowing through it



We talk about the current **through** a component

Current is the rate of flow of charge around the circuit, its units are therefore Coulombs per second A.K.A Ampères (Amps).


definition of current

current is the rate of flow of charge

or

current = charge transferred / time taken

$$I = Q / t$$

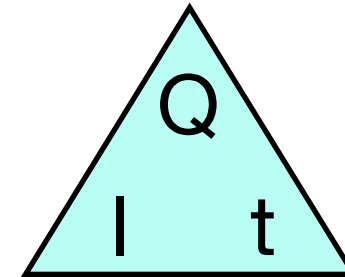

find the charge that passes when a current of 12A flows for 4 minutes...

$$\text{charge} = I \cdot t$$


$$\text{charge} = 12 \cdot 4 \cdot (60)$$

$$\text{charge} = 2,880 \text{ Coulombs}$$

electrons flowing through a wire


time = 0.00 sec
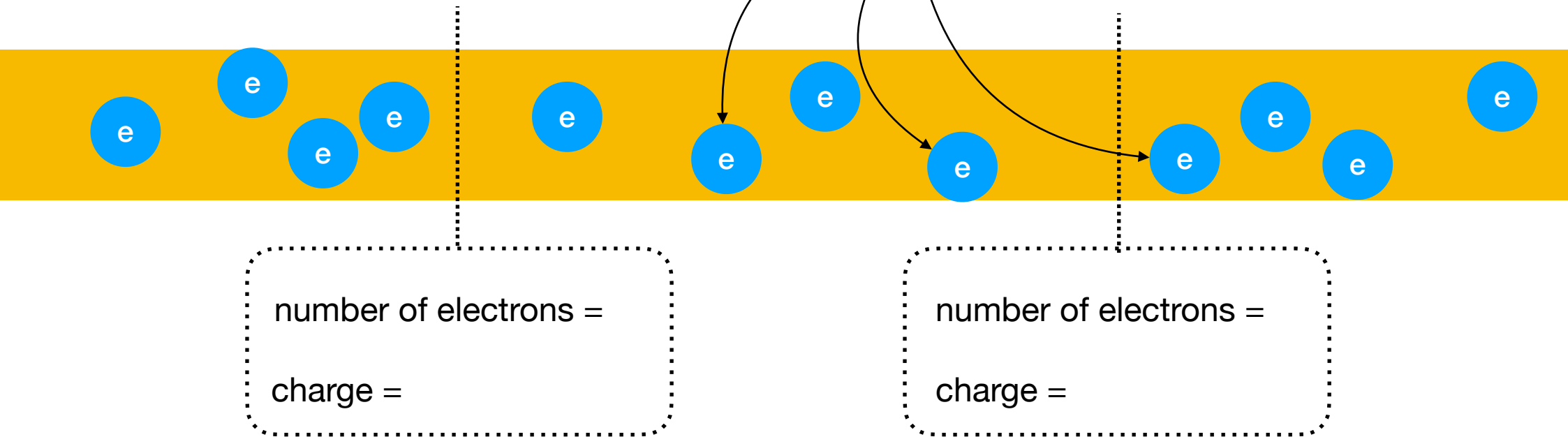
$$e = -1.602 \times 10^{-19} \text{ Coulombs}$$



electrons flowing through a wire

time = 2.00 sec


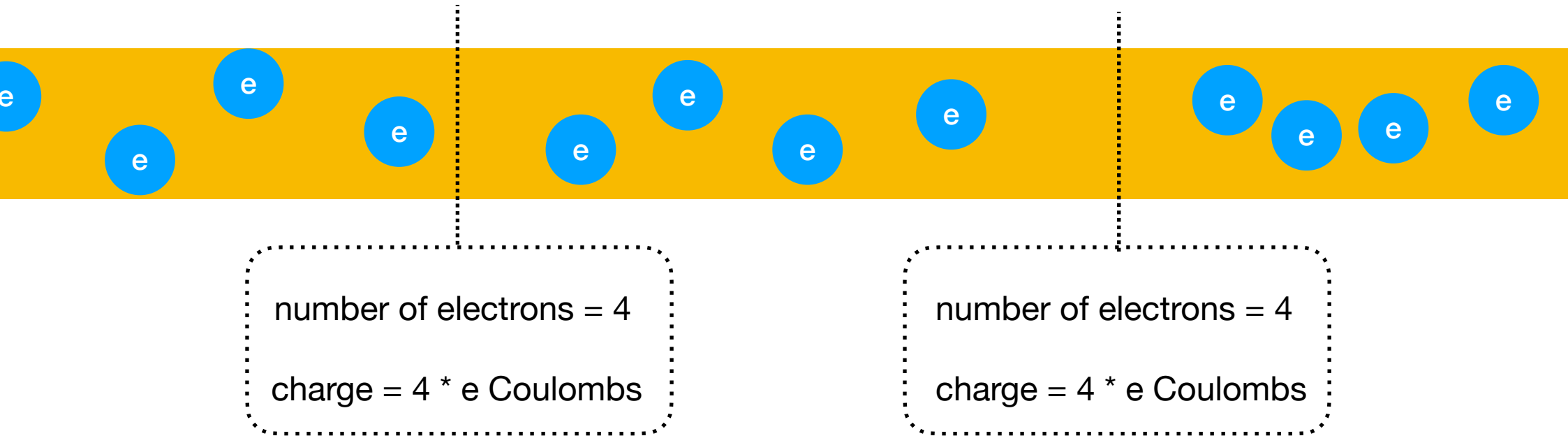


so the current is $4 * e / 2$ Amps

Normally the number of electrons is enormous, not 4.

Current

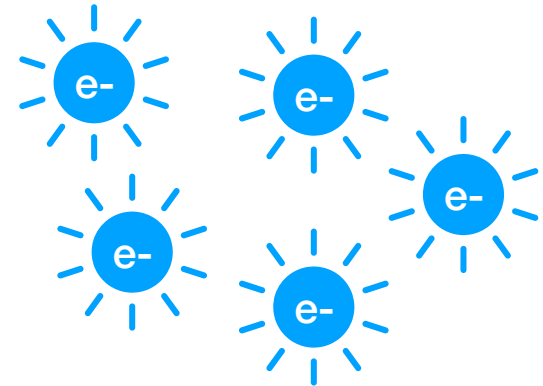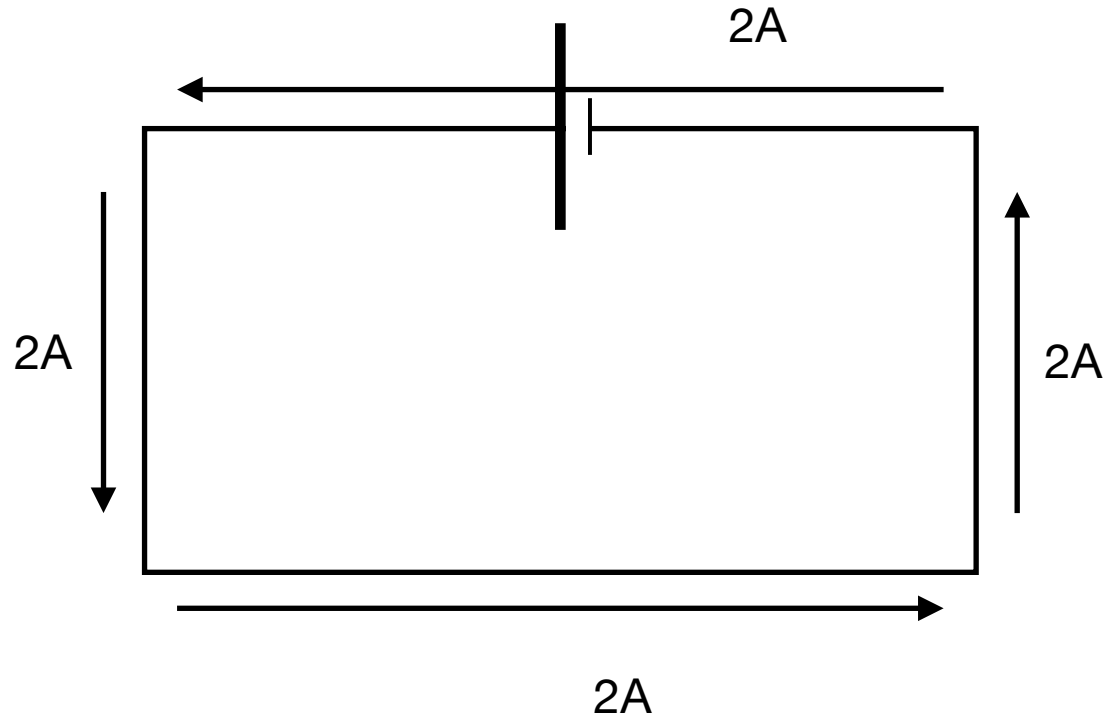
Current doesn't bunch up or spread out, it's incompressible



electrons repel each other because they all have the same charge.

the junction rule

Kirchoff's first law

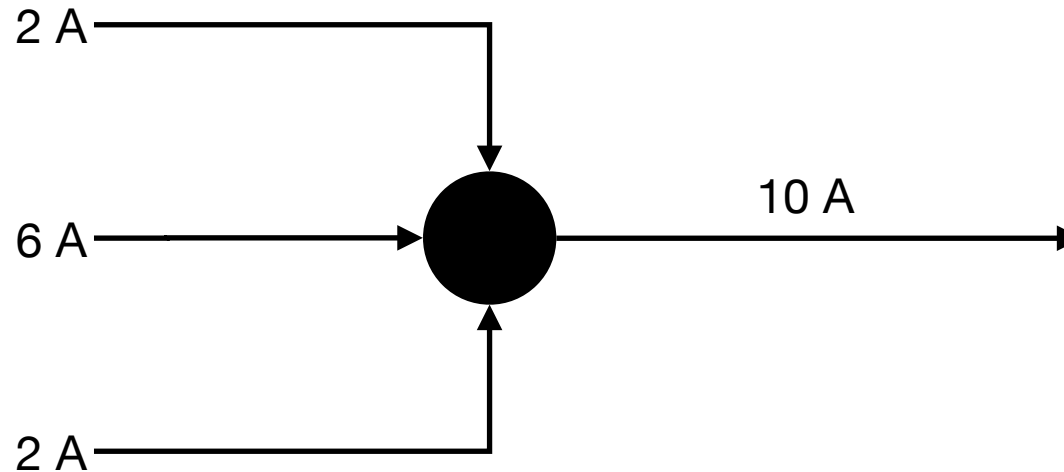

current into a junction = current out


Voltage (V)

Voltage pushes charge around a circuit.

Voltage is the amount of energy each Coulomb of charge gets when it passes through the battery, its units are Joules per Coulomb A.K.A Volts.


The voltage across a component like a resistor is how many Joules each Coulomb of charge loses when it passes through it.

a voltmeter
shows the
voltage across
it

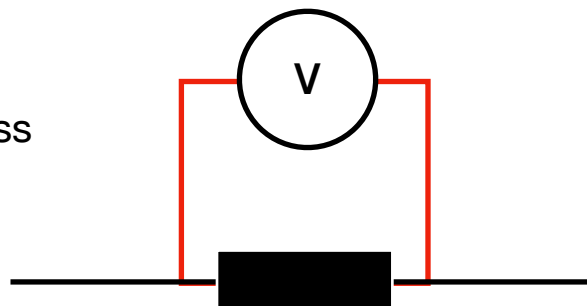


'potential difference' is another
name for voltage

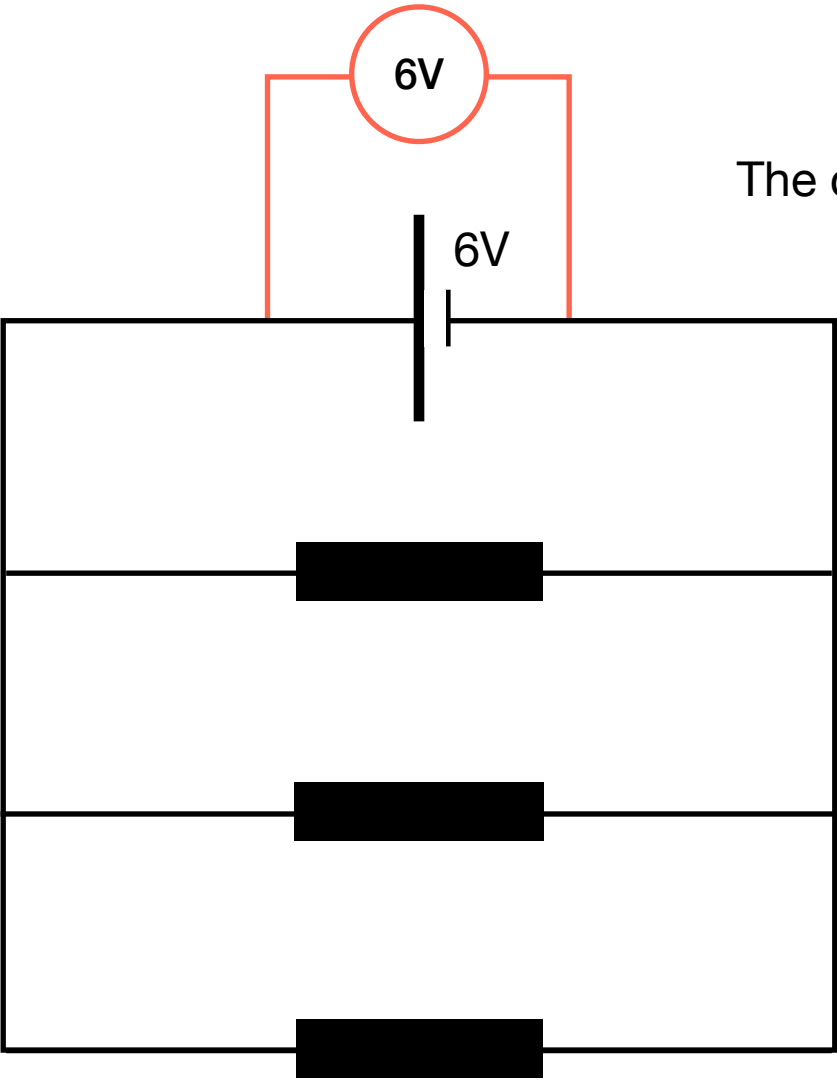
We talk about the voltage **across** a component



The cell voltage is 6V

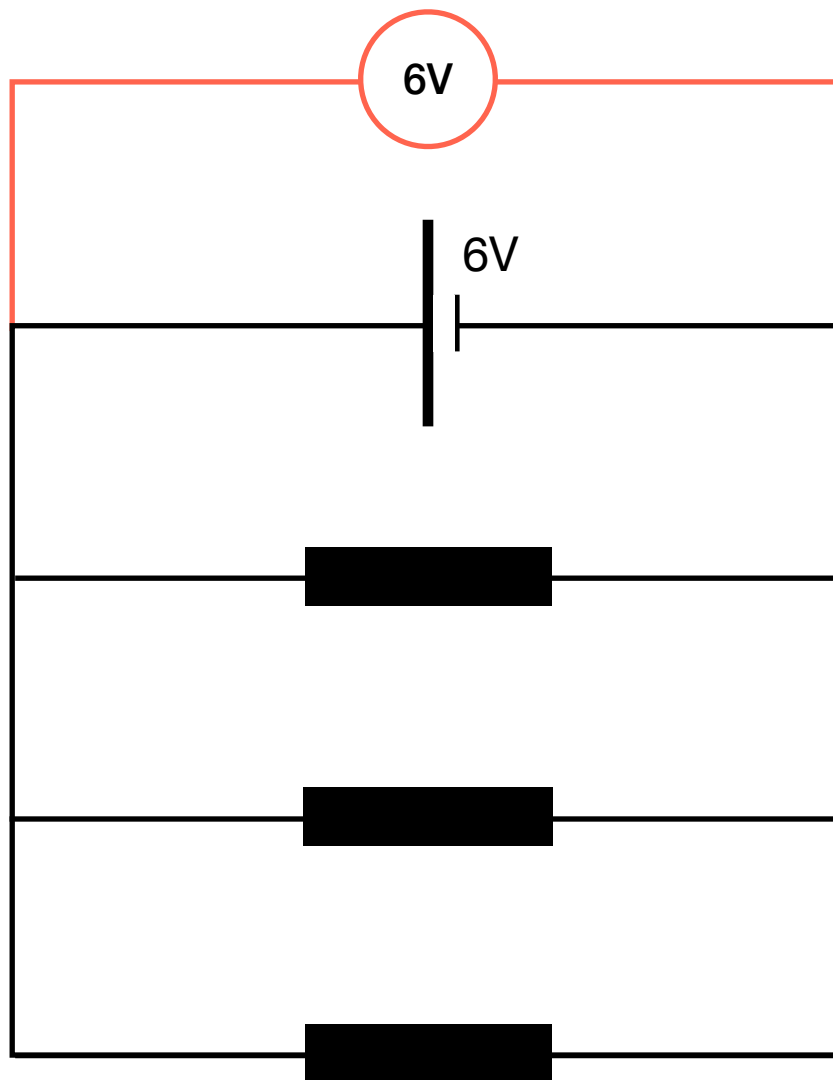


no change

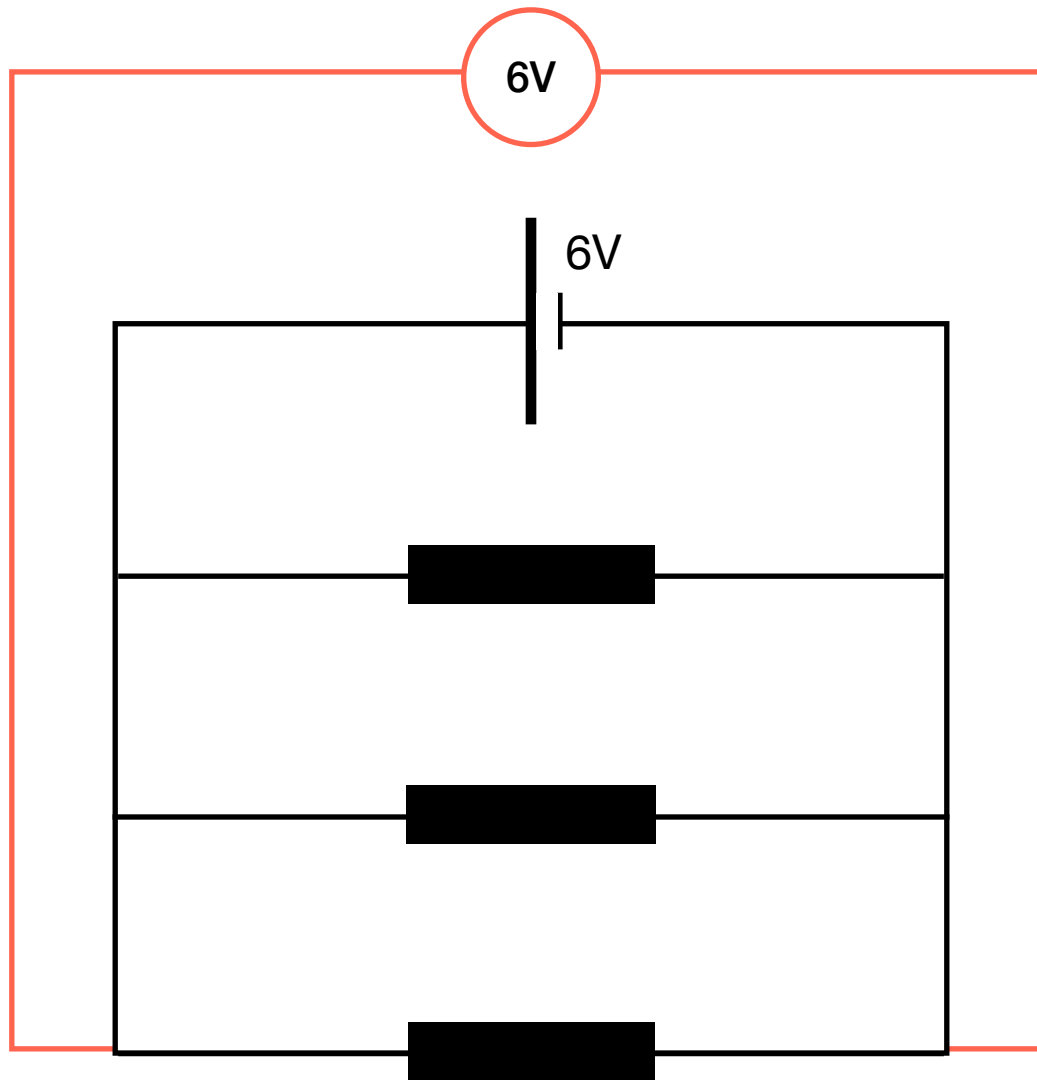

still 6V because the
voltmeter is still
connected to either
side of the cell

Ohm's Law

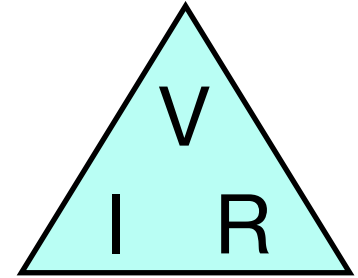

Voltage across a component

Current through a component

Resistance of the component

$$V = I R$$


Volts
a.k.a
Joules / Coulomb

Amps
a.k.a
Coulombs / second


Ohms

The voltage **across** something is equal to the current **through** it times its resistance.

Example

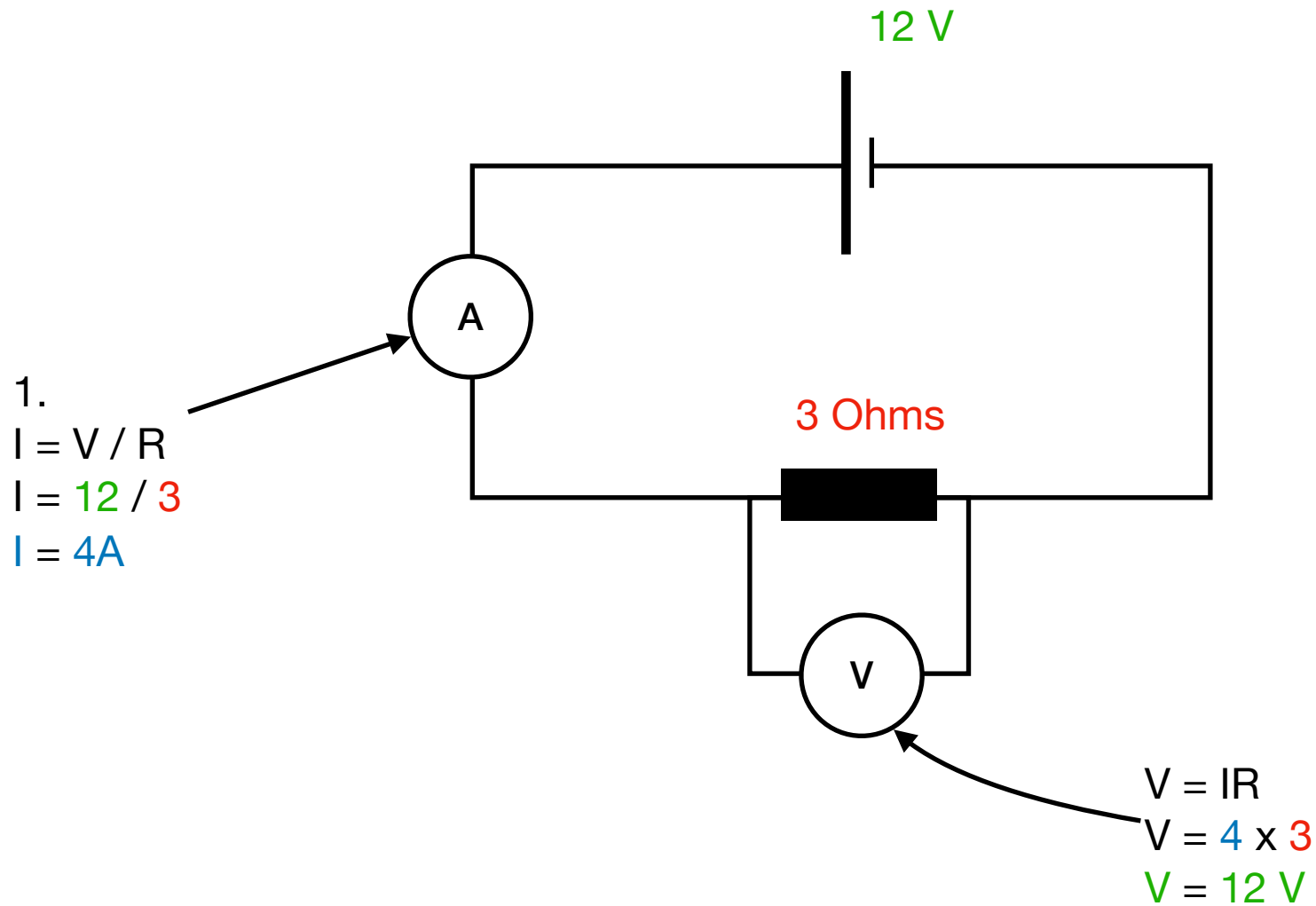

resistors in series

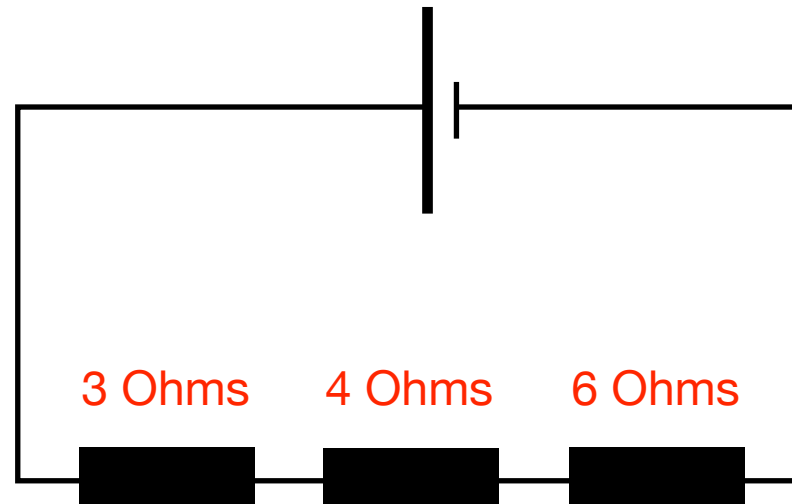

These are in **series**; one after the other.
The voltage across each may differ
but the current through each is the same.

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$\text{Total resistance} = 3 + 4 + 6 = 13 \text{ Ohms}$$


Series Example

2) Ohm's law:

$$I = V/R$$


$$I = 18/80$$

$$I = 0.225 \text{ A}$$

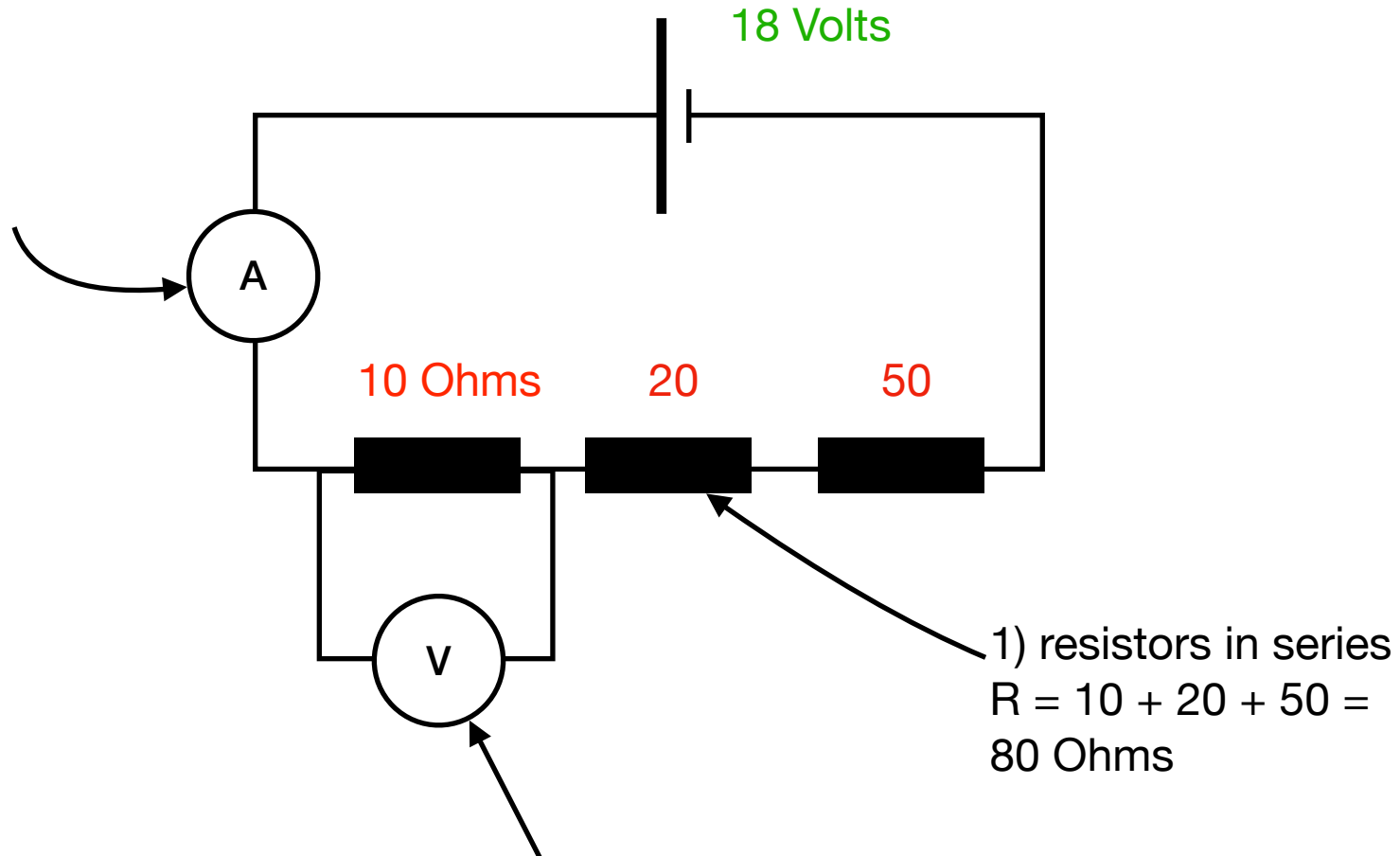


3) Therefore voltage = $IR = 0.225 \times 10 = 2.25 \text{ V}$

Series Example

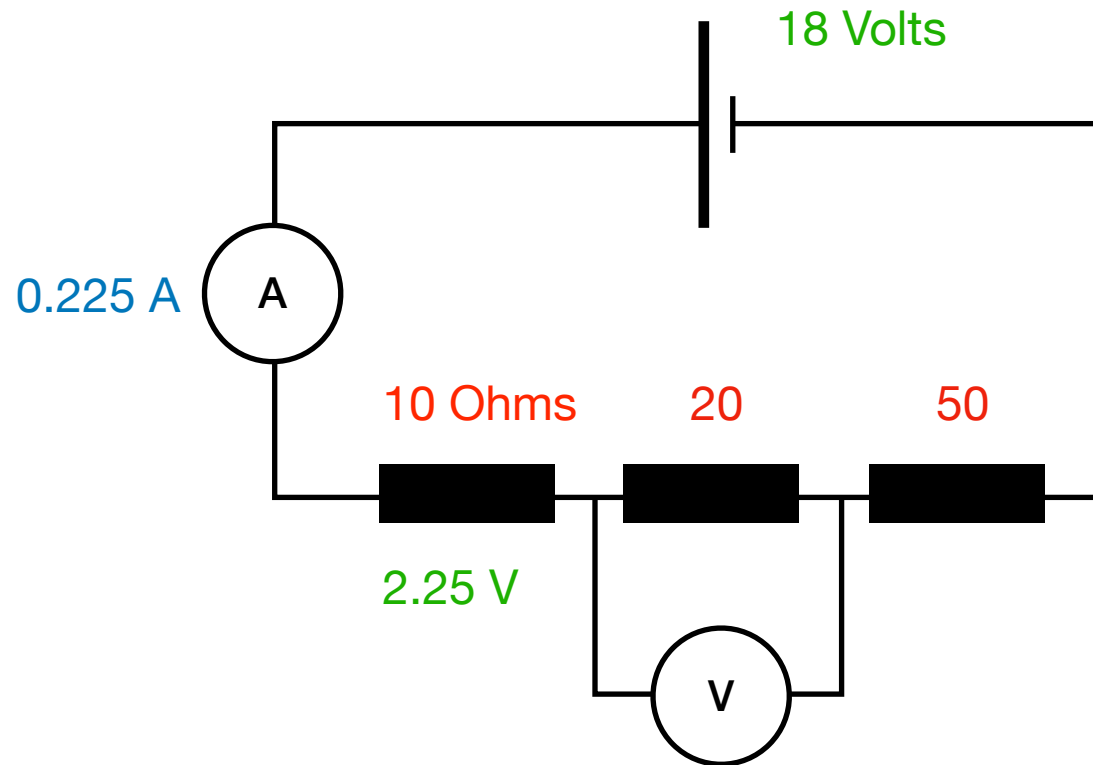


$$V = IR = 0.225 * 20 = 4.5 \text{ V}$$

Series Example

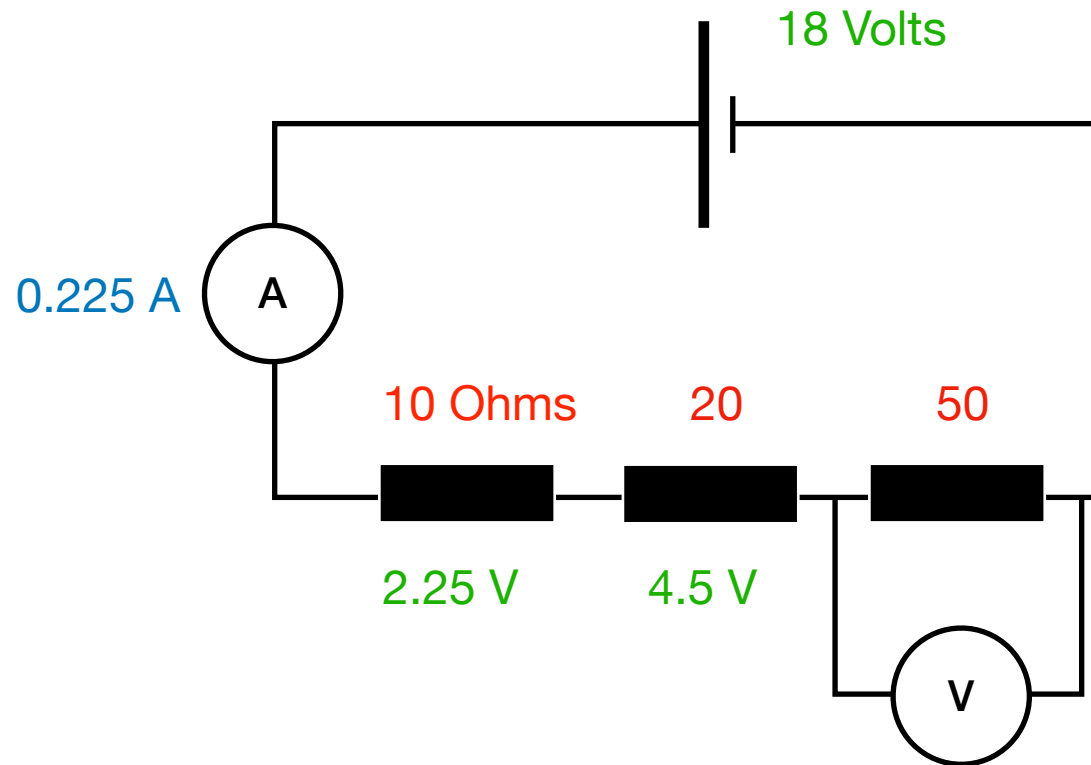

$$V = IR = 0.225 * 50 = 11.25 \text{ V}$$


Series Example

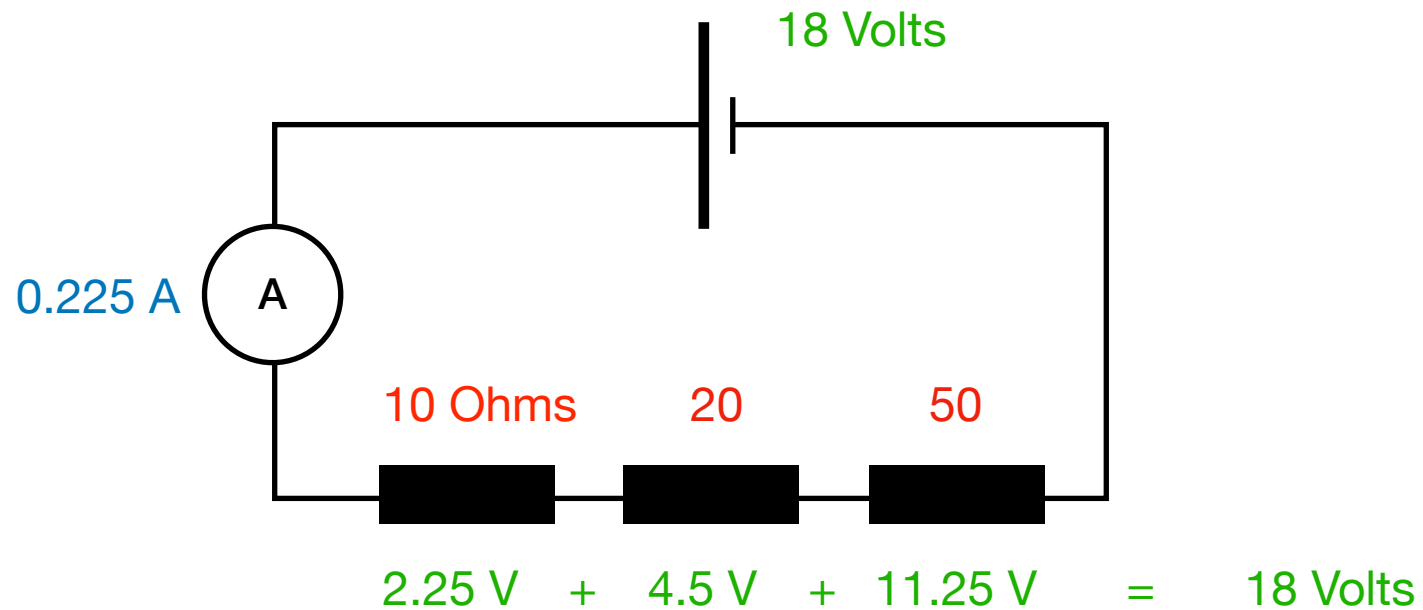

around any closed loop the sum of the battery voltages = the sum of the IR


Potential Divider

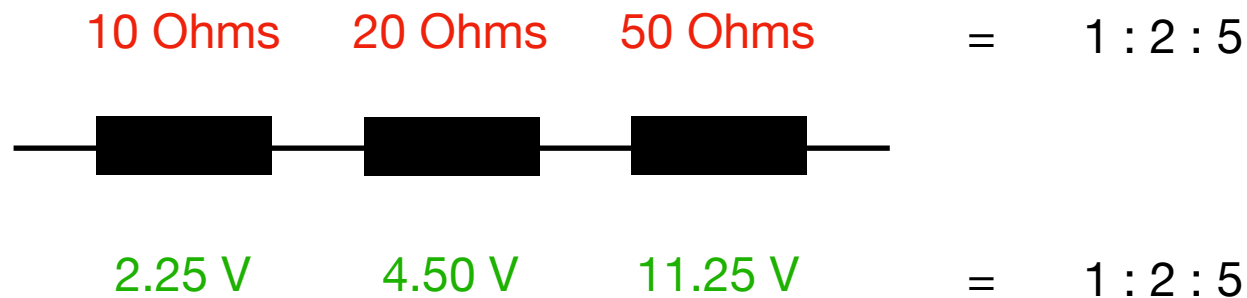In this example we have found that bigger resistances get bigger voltages.



a bunch of resistances in series is called a potential divide circuit and there's a useful equation...

Potential Divider

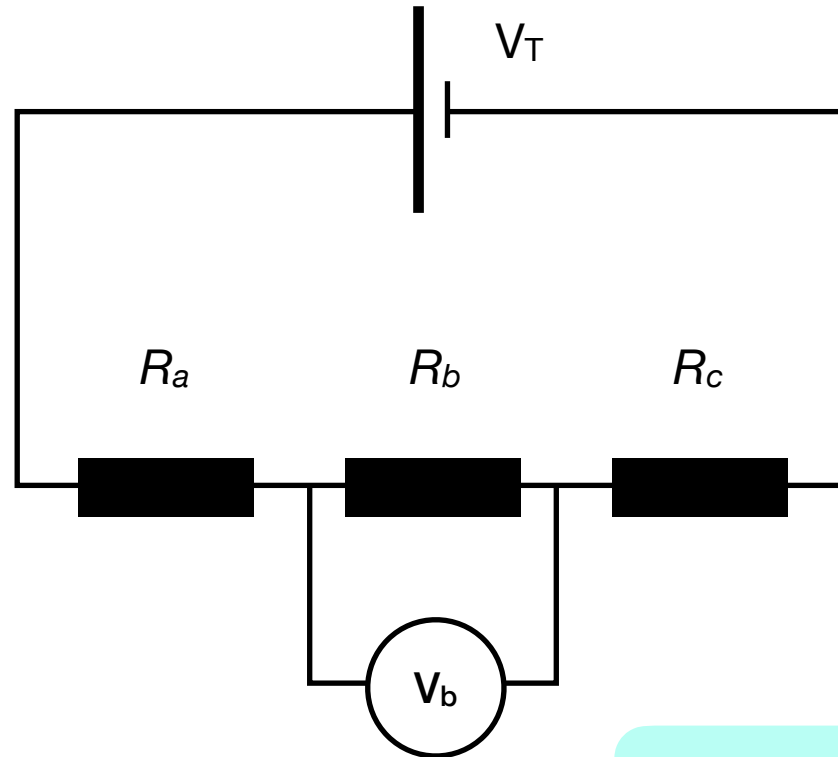


$$V_b = \frac{R_b}{R_T} V_T$$

Potential Divider

a simpler example


$R_t = 60 \text{ Ohms}$

Voltage = 18V

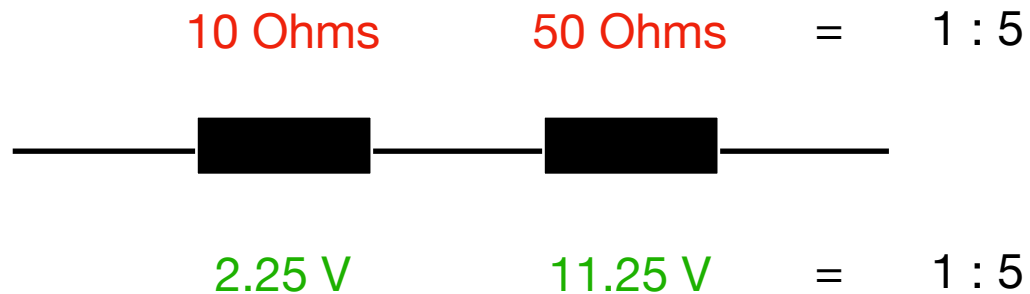

a bunch of resistances in series is called a potential divide circuit and there's a useful equation...


Potential Divider

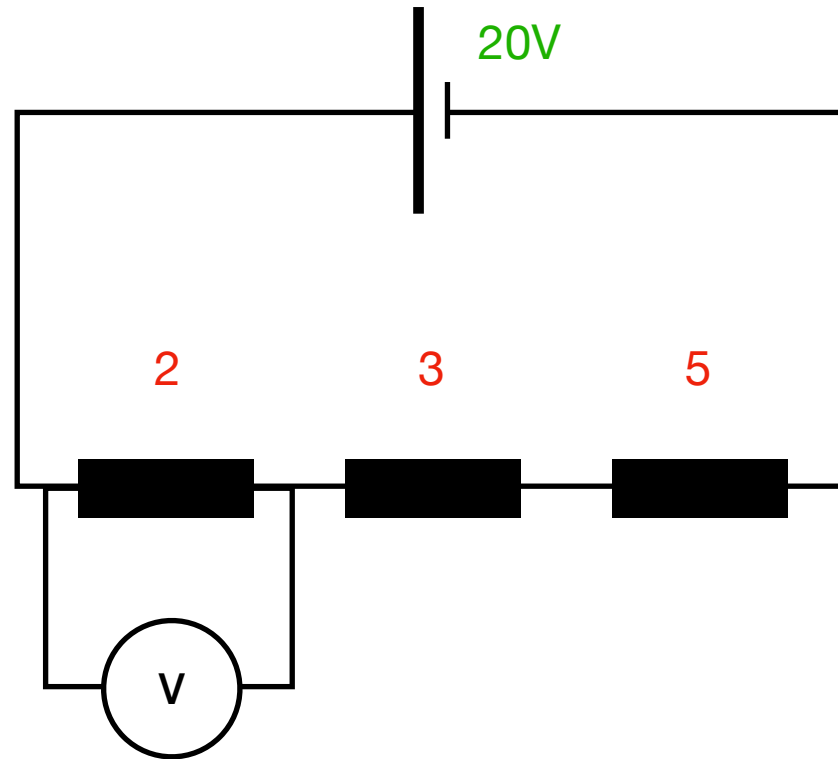

$$V_b = \frac{R_b}{R_T} V_T$$


$$2/10 * 20 = 4V$$

Potential Divider

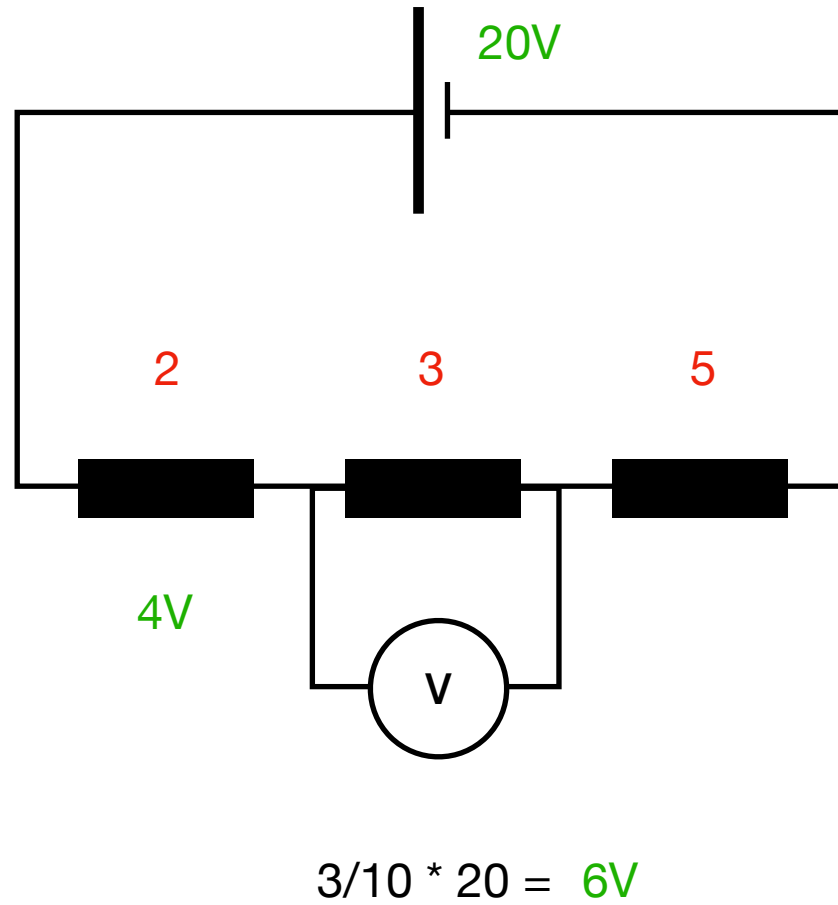

$$V_b = \frac{R_b}{R_T} V_T$$


Potential Divider

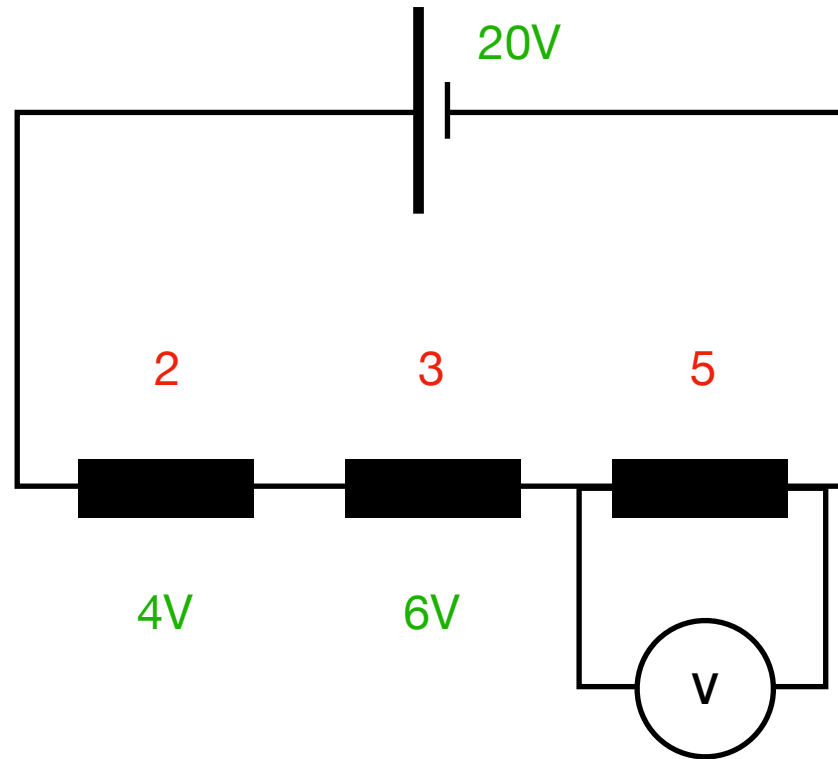

$$5/10 * 20 = 10V$$


$$V_b = \frac{R_b}{R_T} V_T$$

Potential Divider

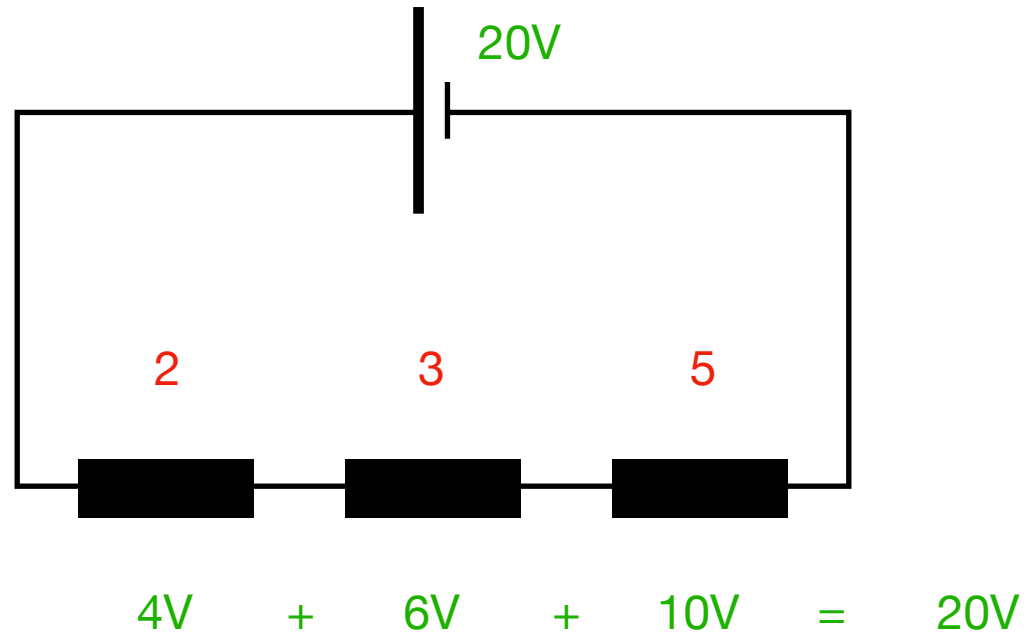

$$V_b = \frac{R_b}{R_T} V_T$$

resistors in parallel

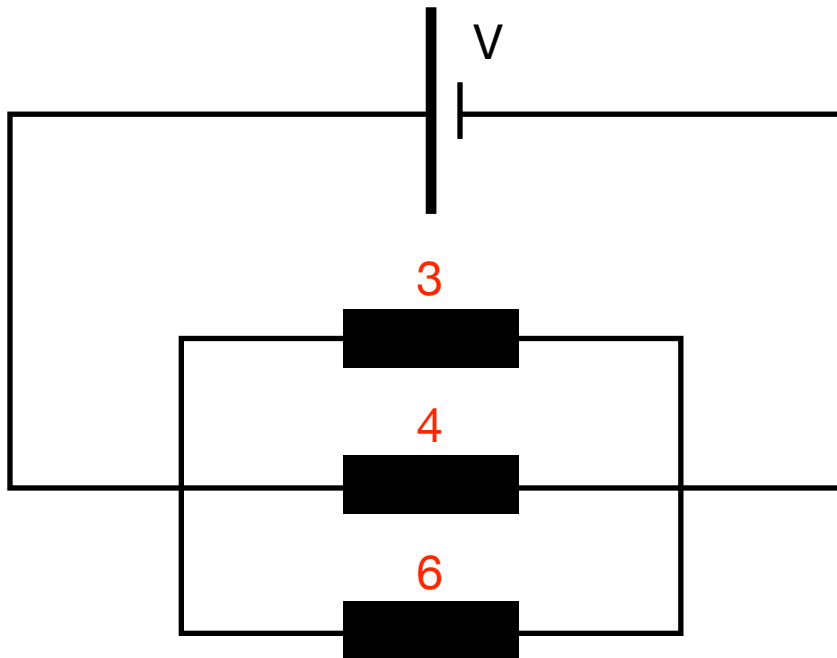


These are in **parallel**.

The voltage across each is the same but the current through each may differ.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$$\frac{1}{R_T} = \frac{1}{3} + \frac{1}{4} + \frac{1}{6} = \frac{4}{3} \Omega$$

Parallel Example

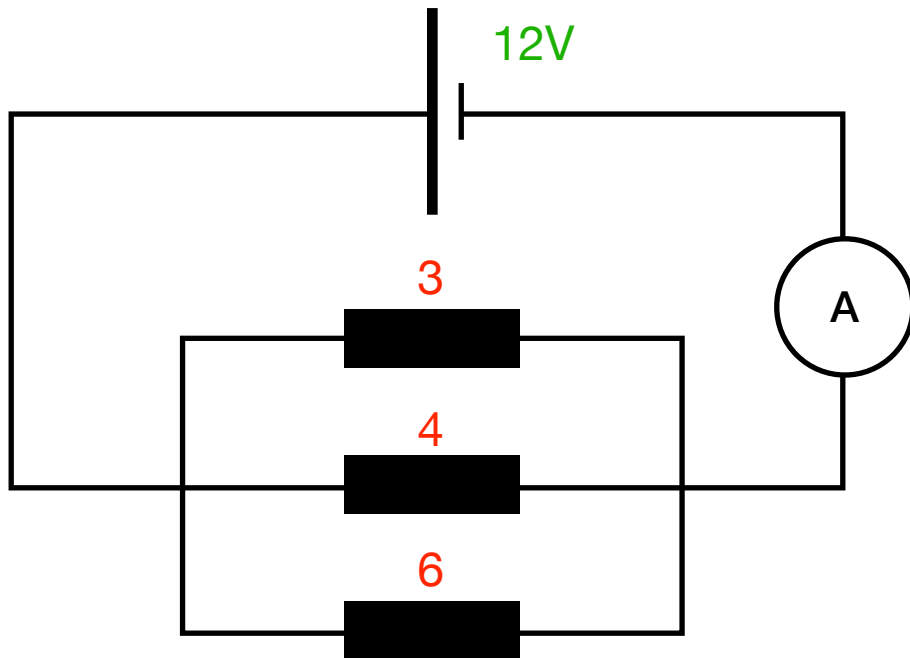

1) $R_T = 4/3 \text{ Ohms}$

2)

$$I = V/R$$

$$I = 12 / (4/3)$$

$$I = 9A$$

3) Finding the current through each resistor is easy


$$I = V/R = 12/3 = 4A$$

$$I = V/R = 12/4 = 3A$$

$$I = V/R = 12/6 = 2A$$


N.B these add to 9A, the total current.

Equations

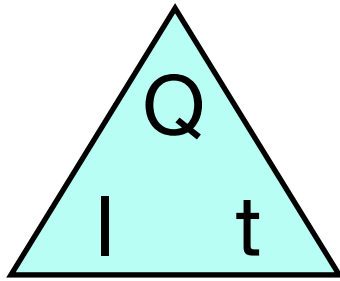

Charge transferred = Current * time

C A s

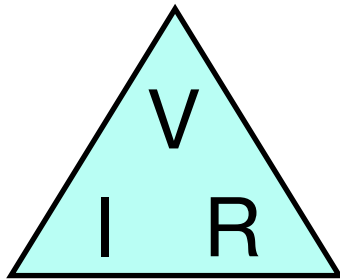

Voltage = Current * Resistance

V A Ohms

$$R_T = R_1 + R_2 + R_3 + \dots$$

$$V_b = \frac{R_b}{R_T} V_T$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$