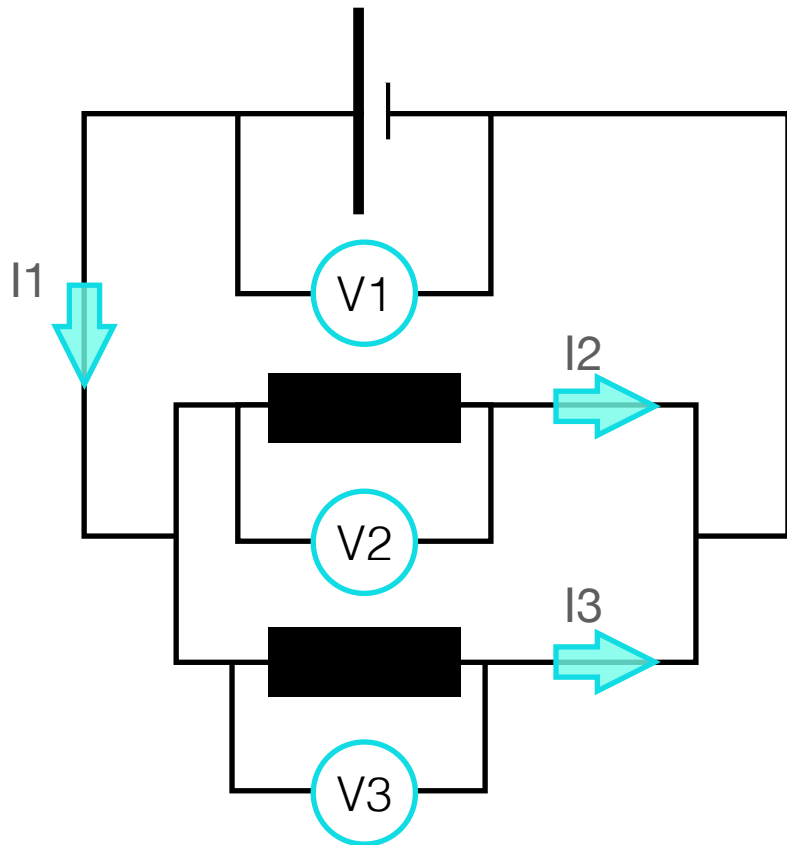



series and parallel circuits



$I_1 =$ _____ $V_1 =$ _____

$I_2 =$ _____ $V_2 =$ _____

$I_3 =$ _____ $V_3 =$ _____

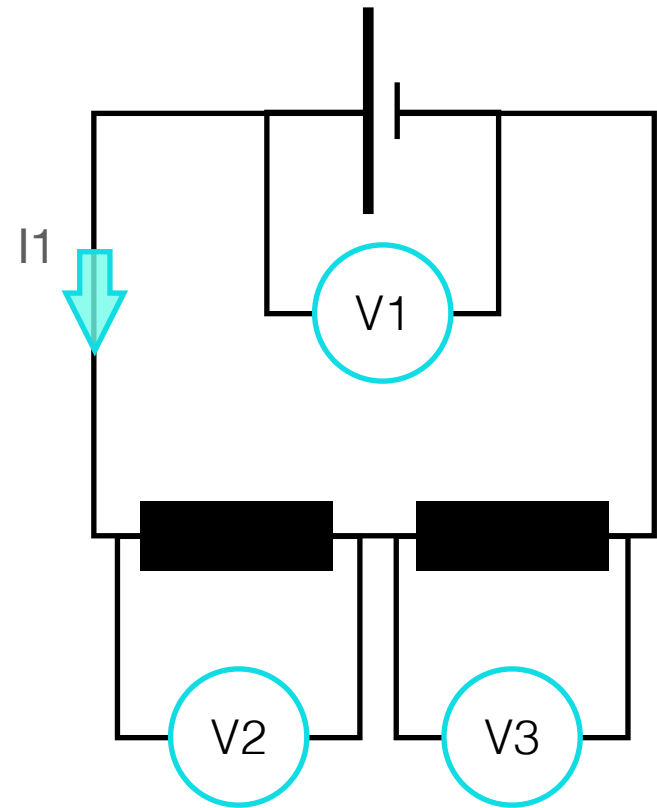

$I_1 =$ _____

$V_1 =$ _____

$V_2 =$ _____

$V_3 =$ _____